


Updates to design of Panny GH1 remote shutter control.

Note that circuit below at

<http://ranger9.net/?p=906>


did not work for new Gh1 ver 3 firmware. After substantial amount of trial and error tinkering I discovered the following modifications make it work. Apparently voltage must be increased to 2.5 V when plugged in otherwise the firmware did not recognize that it was plugged in.

### Original design would not work

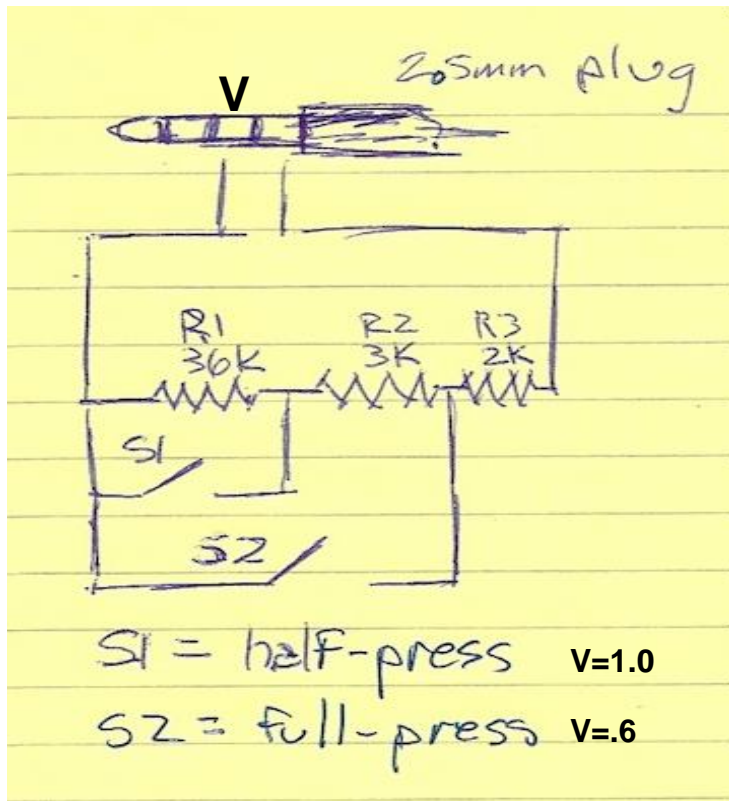

no button press v=2.0

### Modified design

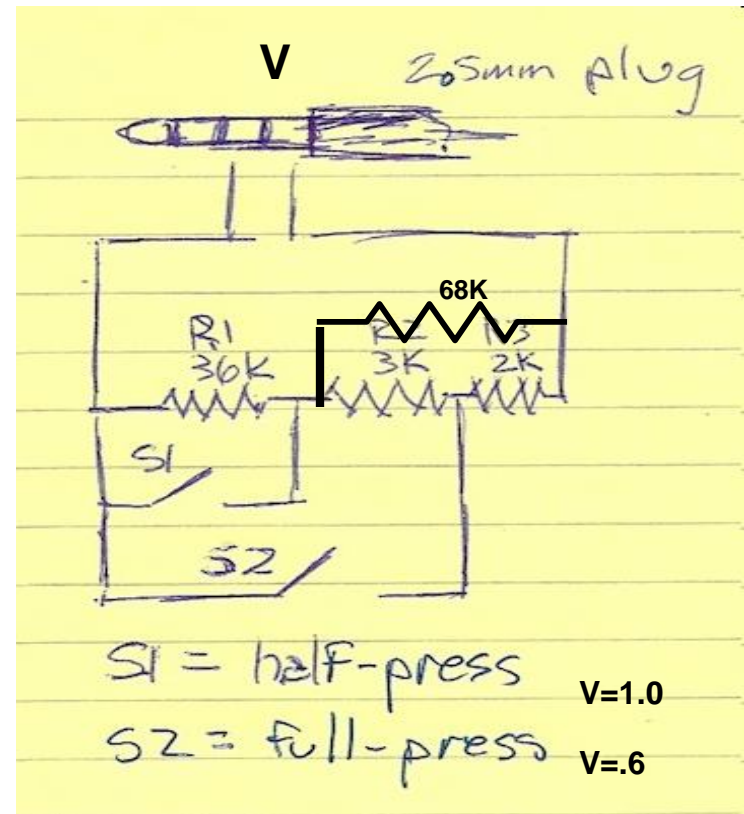

no button press v=2.5